



Design and Implementation of a 16-bit Single-Cycle RISC CPU Using Logisim-Evolution 3.9.0

King Fahd University of Petroleum and Minerals

COE 301: Computer Architecture & Assembly Language (Term 242)

10th May 2025

Name: Amer Almutairi

ID: 202169770

Section#: 53, Monday


Abstract

This report describes the design, implementation, and verification of a 16-bit, five-stage pipelined RISC processor using Logisim-evolution . The processor implements a small RISC-style ISA with R-type, I-type, and J-type instructions, including arithmetic, logic, memory, branch, and bit-reversal operations. We detail the Datapath, control logic, forwarding and hazard-detection units, test programs, and team organization.

Contents

1	Datapath Components	4
1.1	Register File	4
1.2	Arithmetic & Logic Unit (ALU)	5
1.3	Sign/Zero Extender	6
1.4	Program Counter (PC) Logic	7
1.5	Data Memory	7
2	Control Logic	9
2.1	Control Table	9
2.2	Control Signals	9
3	Simulation and Testing.....	10
4	Conclusion	16
5	References & Installing Logisim-evolution 3.9.0	16

1 Datapath Components

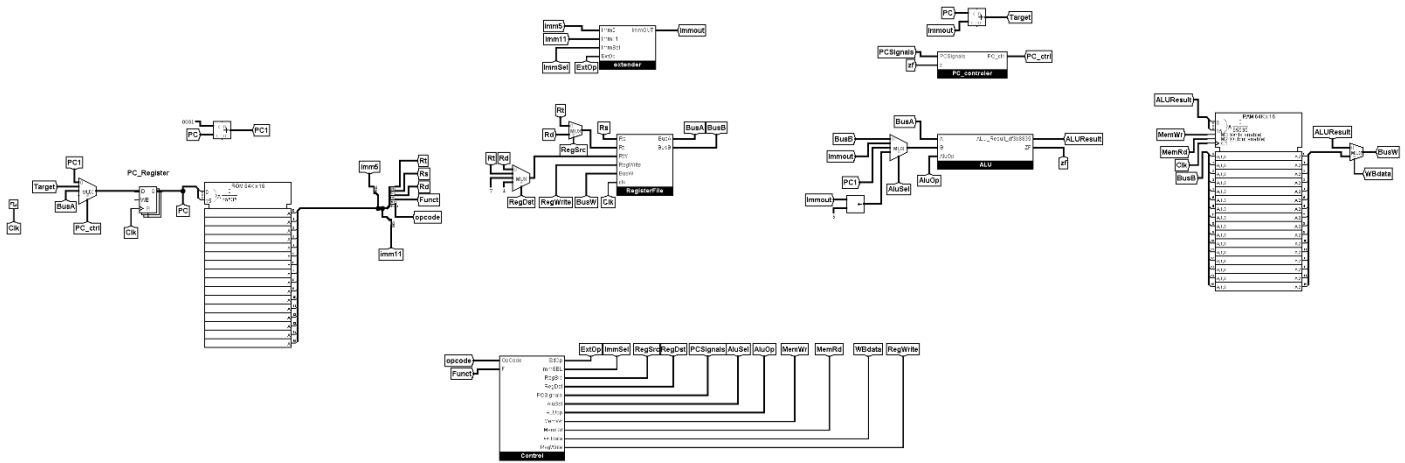


1.1 Register File

R1–R7 (16 bits each), R0 hardwired to 0.

On the rising edge of Clock, if RegWrite = 1, the 16-bit WriteData is written into the register indexed by RW.

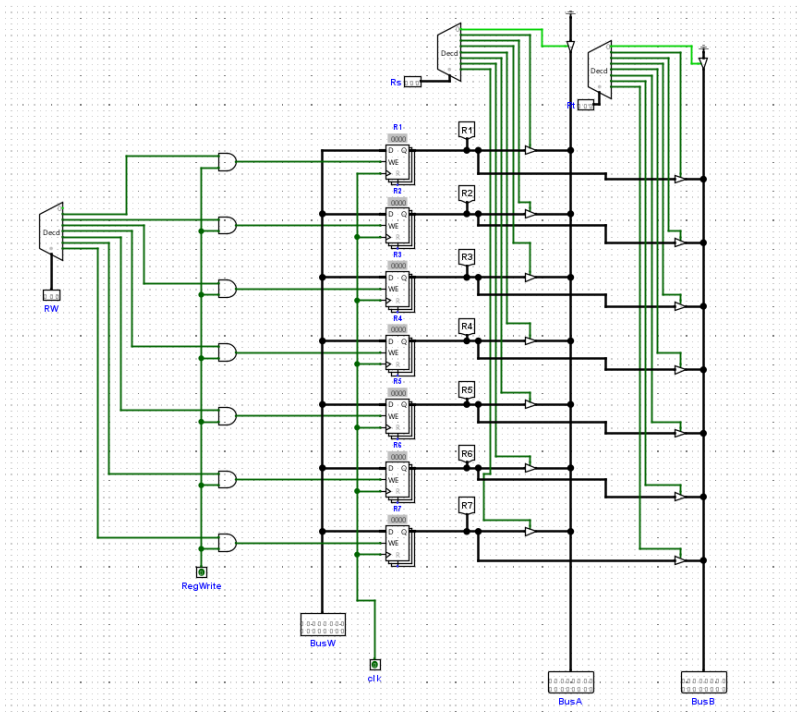At all times, the contents of registers RS and RT appear on BusA and BusB, respectively.



Input:


- RS (3 bits): address of source register A
- RT (3 bits): address of source register B
- RW (3 bits): address of destination registers
- WriteData (16 bits): data to be written
- RegWrite (1 bit): write-enable control

Output:

BusA (16 bits): data read from RS

BusB (16 bits): data read from RT

1.2 Arithmetic & Logic Unit (ALU)

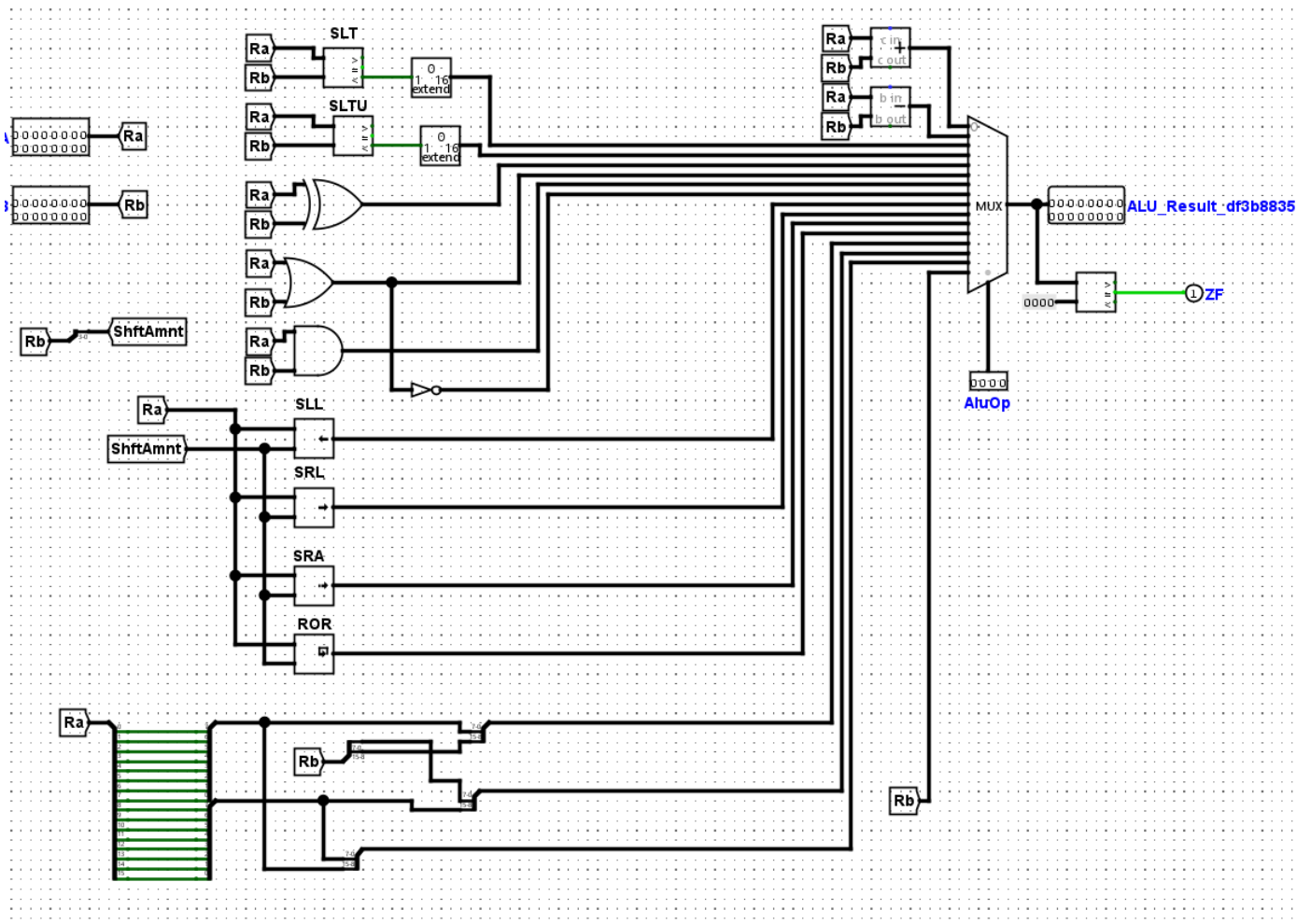

Input:

- A (16 bits): operand A from BusA
- B (16 bits): operand B or immediate (via ALUSrc)
- ALUOp (4 bits): selects operation


Output:

- ALUResult (16 bits): result
- Zero (1 bit): (ALUResult==0) flag

Supports the 16-bit operations listed in the spec, including:

- **Arithmetic:** ADD, SUB
- **Shifts/Rotates:** SLL, SRL, SRA, ROR
- **Comparisons:** SLT (signed), SLTU (unsigned)
- **Reversal:** REVA, REVL, REVH
- **Bitwise:** AND, OR, XOR, NOR



1.3 Sign/Zero Extender

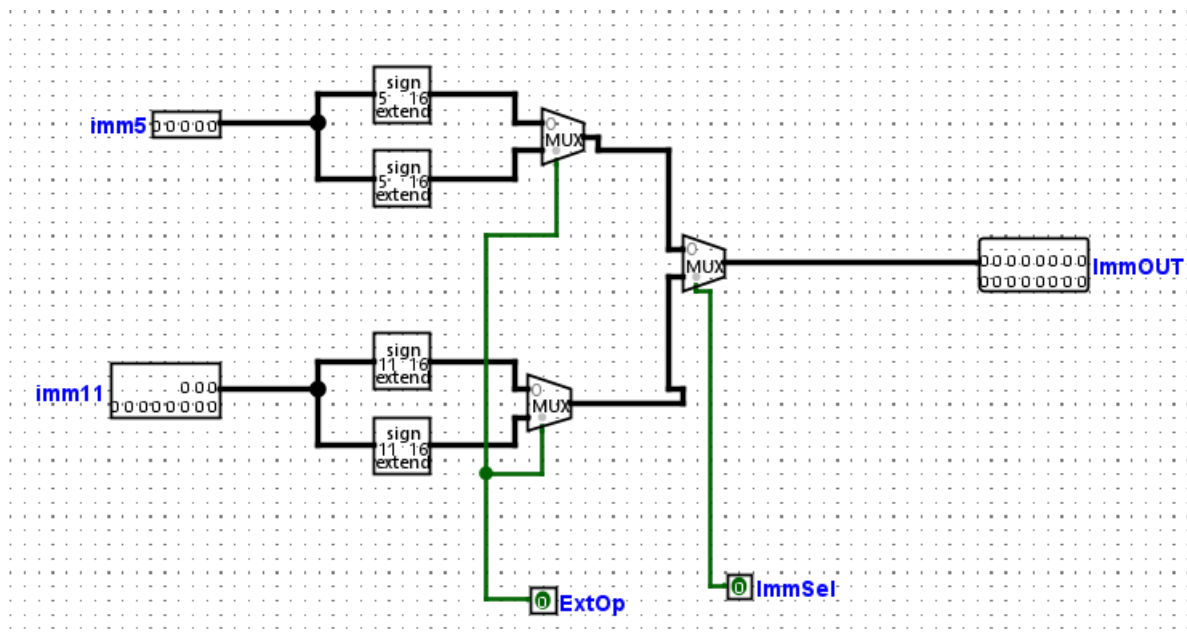

I-type: Sign-extends 5-bit immediates for most instructions; zero-extends for ANDI/ORI/XORI.

J-type: Zero-extends 11-bit immediates for J, JAL, and LUI.

1.4 Program Counter (PC) Logic

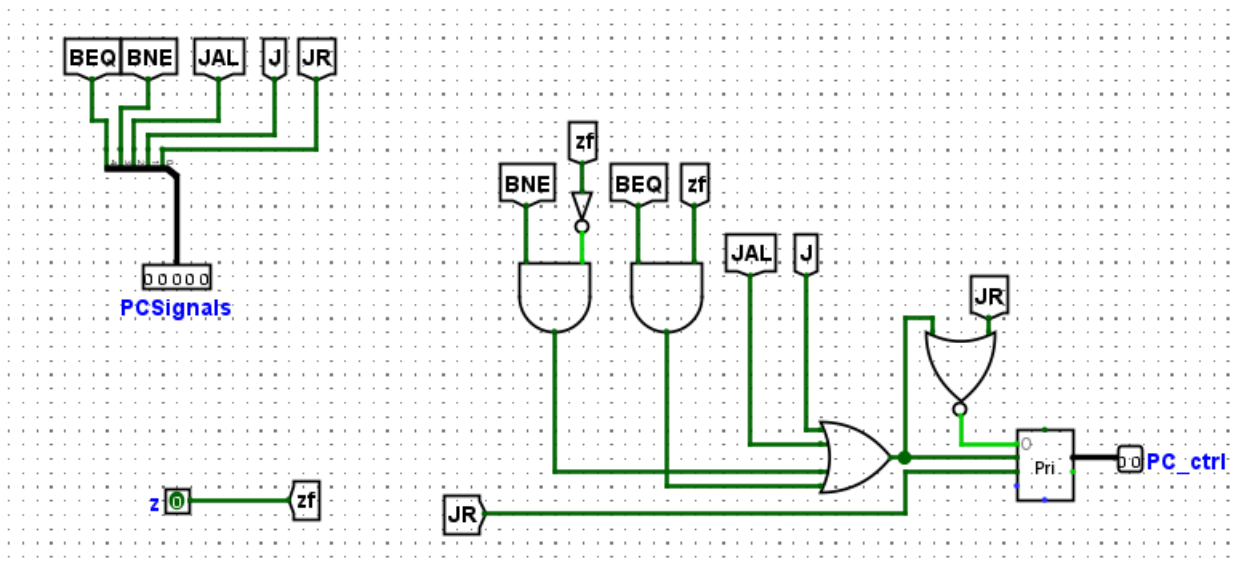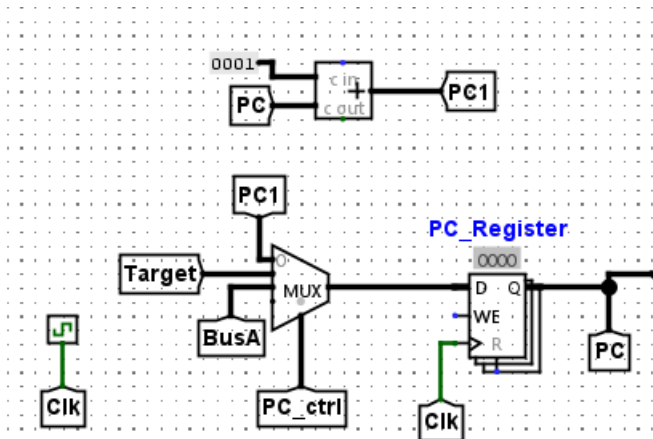

Computes NextPC:

PC+1 adder for sequential fetch.


Branch adder: $PC_{in} + \text{sign_extend}(\text{Imm5})$ for BEQ/BNE.

Jump adder: $PC_{in} + \text{zero_extend}(\text{Imm11})$ for J/JAL.

MUX network selects next PC based on Branch & Zero, Jump, or fall-through

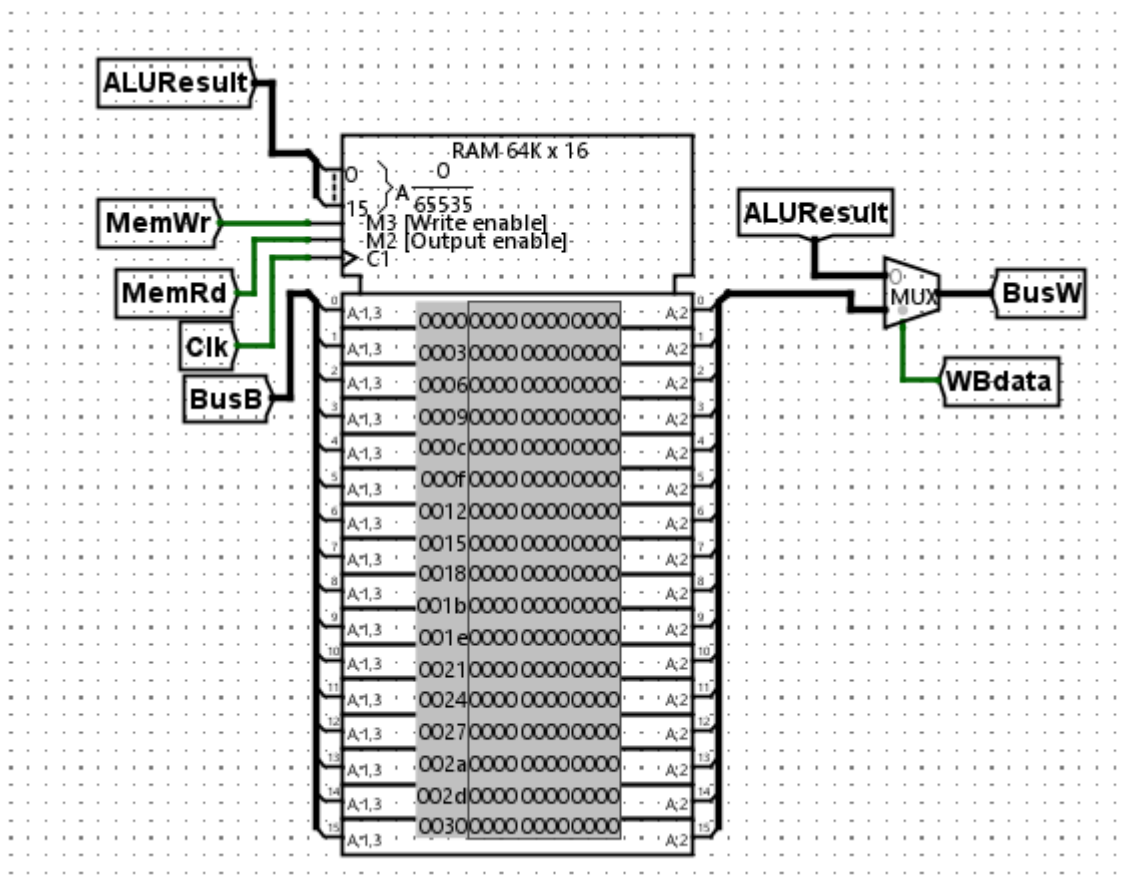1.5 Data Memory

Implements a $64\text{ K} \times 16\text{-bit}$ RAM. On the rising edge of Clk, if MemWr=1 it writes WriteData into the cell indexed by Addr. If MemRd=1, the contents at Addr drive ReadData, which is then selected by the WB-stage MUX as WBdata when appropriate.




Inputs:

- Addr (16 bits): address from ALUResult
- WriteData (16 bits): data from BusB
- MemWr (1 bit): memory-write enable
- MemRd (1 bit): memory-read enable

Outputs:

- ReadData (16 bits): data output when MemRd=1 (goes to BusW via MUX)

2 Control Logic

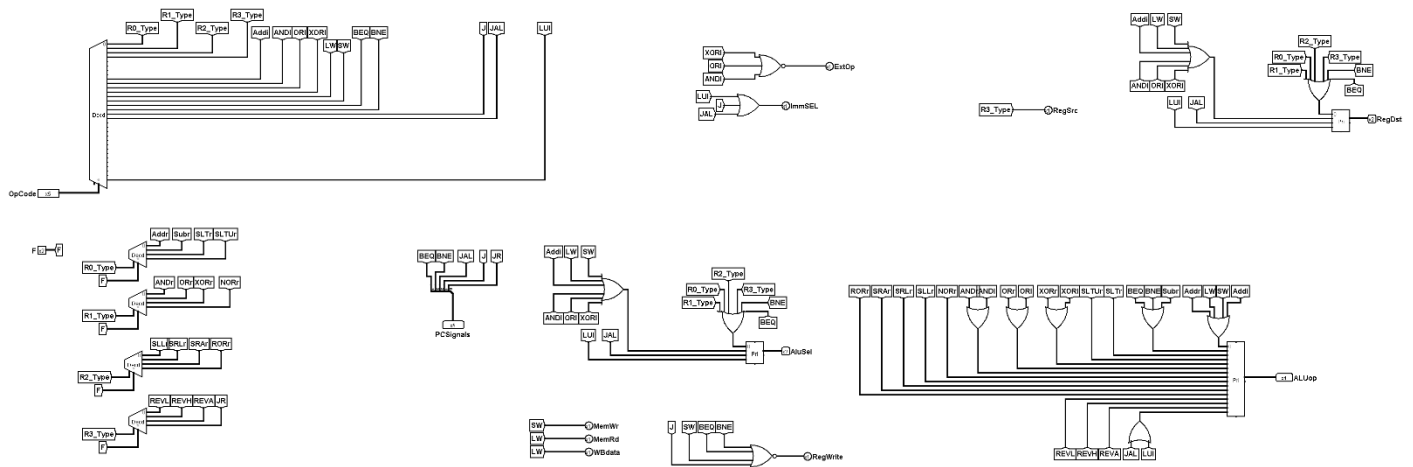

2.1 Control Table

INSTR.	OP[4:0]	F[1:0]	REGDST	ALUSRC	MEMREAD	MEMWRITE	MEMTOREG	REGWRITE	BRANCH	JUMP	ALUOP
ADD	00000	00	1	0	0	0	0	1	0	0	0000
SUB	00000	01	1	0	0	0	0	1	0	0	0001
LW	01100	–	0	1	0	1	1	0	0	0010	0010
SW	01101	–	–	1	0	1	–	0	0	0	
BEQ	01110	–	–	0	0	0	–	0	1	0	0110
JAL	10001	–	0	0	0	0	0	1	0	1	xxxx
JR	00011	11	–	0	0	0	–	0	0	1	xxxx


2.2 Control Signals

SIGNAL	SOURCE LOGIC	DESCRIPTION
RegDst	3-way priority MUX selecting one hot from: - R3_Type (all R-type non-shift/reverse) - R1_Type (shift/SLT group) - R2_Type (reverse group) - LUI, JAL	Chooses destination register index: '00'=Rt (I-type), '01'=Rd (R-type), '10'=R3 field, '11'=link reg
RegWrite	OR of its "write-back" instruction lines: 'ADDI' ∨ 'LW' ∨ 'SW' ∨ 'BEQ'/'BNE' ∨ 'J' ∨ 'SW' (see bottom-left OR-gate)	Enables register file write on WB stage
ALUSrc	OR-gate combining I-type data-immediate ops: 'ADDI' ∨ 'LW' ∨ 'SW'	Selects ALU B-input source: BusB (0) vs. immediate (1)
MemRead	Directly from the 'LW' decode line	When high, Data Memory drives its output onto **ReadData**
MemWrite	Directly from the 'SW' decode line	When high (on clock edge), BusB is written into Data Memory at ALUResult address
MemToReg	Equals **MemRead** (wired)	Selects WB-stage MUX: ALUResult (0) vs. ReadData (1)
Branch	OR-gate of 'BEQ' and 'BNE' decode lines	Indicates conditional branch; used with **Zero** flag to choose PC target
Jump	OR-gate of 'J', 'JAL', and 'JR' decode lines	Indicates unconditional jump (PC←target or PC←Rs)
PCSrc[2:0] (encoded)	3-bit bus from the small "PCSignals" decoder (BEQ/BNE/J/JAL/JR)	Controls the 4-way PC MUX: +1 (000), branch (001), jump-imm (010), JR (011)
ExtOp	OR-gate of 'XORI', 'ORI', and 'ANDI'	When high, forces zero-extension of the 5-bit immediate
ImmSel	OR-gate of 'LUI' and 'JAL'	When high, selects 11-bit zero-extended immediate instead of sign-extended 5-bit
ALUOp[3:0]	16-to-1 MUX with inputs driven by each decoded R/I-type operation line (ADD, SUB, AND, OR, ... REVH)	Chooses which internal ALU sub-operation to perform

3 Simulation and Testing


The Following Code Blocks are testing the whole CPU Instructions Set

#	Assembly Code	Code(Hex)	
0	addi \$1, \$0, 5	4141	R1 = 0005
1	or \$2, \$1, \$0	0A88	R2 = 0005
2	ori \$3, \$0, 7	51C3	R3 = 0007
3	xor \$4, \$3, \$2	0D1A	R4 = 0002
4	and \$5, \$3, \$4	095C	R5 = 0002
5	nor \$6, \$0, \$4	0F84	R6 = FFFD
6	andi \$7, \$3, 5	495F	R7 = 0005

 


is being tested as illustrated in this example with data dependencies

7	add \$1, \$1, \$2	004A	R1 = 000A
8	sub \$2, \$1, \$3	028B	R2 = 0003
9	slt \$3, \$6, \$2	04F2	R3 = 0001
A	sltu \$4, \$6, \$2	0732	R4 = 0000
B	xori \$5, \$2, 5	5955	R5 = 0006

 


C	sll \$1, \$1, \$2	104a	R1 = 00A0; R1 = 0050
D	srl \$3, \$6, \$2	12f2	R3 = 0FFF; R3 = 1FFF
E	sra \$4, \$6, \$2	1532	R4 = FFFF
F	ror \$5, \$3, \$2	175A	R5 = F0FF; R5 = E3FF

 


Result after reaching **0x77a5** in this test below,

10	lui 0x76C	FF6C	R1 = ED80
11	reva \$2, \$1	1C88	R2 = 01B7, R1 = ED80
12	revh \$1, \$2	1A50	R1 = ED80, R2 = 01B7
13	revl \$2, \$1	1888	R2 = 0101, R1 = ED80
14	addi \$2, \$0, 6	4182	R2 = 0006
15	sw \$4, 4(\$2)	6914	Mem[0Ah] = 0xFFFF, R2 = 0006
16	lw \$5, 4(\$2)	6115	R5 = 0FFF
17	sw \$5, 3(\$2)	6895	Mem[09h] = 0xFFFF, R5 = FFFF
18	add \$5, \$5, 0	0168	R5 = FFFF, R6 = FFFD, R7 = 0005
19	xor \$3, \$1, \$1	0CC9	R3 = 0000; Clear R3
1A	bne \$3, \$0, 4	7918	R3 = 0000 = R0, Branch not taken
1B	subi \$3, \$3, 1	47DB	R3 = FFFF (= -1)
1C	beq \$5, \$3, 3	70EB	R5 = R3 = FFFF, Branch taken
1D	addi \$1, \$0, 0	4001	R1 = 0000
1E	bne \$3, \$1, 5	7959	R3 = FFFF (!=R1), Branch taken
1F	beq \$4, \$5, -2	77A5	R4 = FFFF (= R5), Branch taken

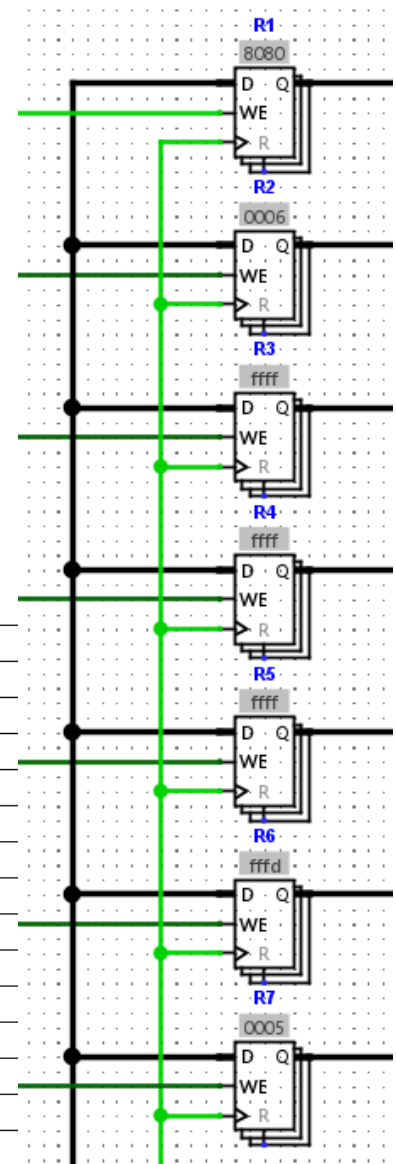

 is being tested as illustrated in this example when the last instruction stores a value that has just been loaded in the instruction before it as shown:



Fibonacci Array

```

    addi $3, $0, 10      # R3 ← loop count (10)
    addi $4, $0, 0       # R4 ← index = 0
    addi $5, $0, 3       # R5 ← value_to_store = 3

loop:  sw $5, 0($2)      # MEM[R2] ← 3
    addi $4, $4, 1       # index++
    addi $2, $2, 1       # pointer++
    bne $4, $3, loop     # if index ≠ 10, repeat

    addi $1, $0, 0       # R1 ← output_ptr_base (start addr)
    jal fib              # call fib(), R7 ← return addr
    j exit              # simple halt

fib:   xor $2, $2, $2     # R2 ← counter = 0
    addi $3, $0, 9       # R3 ← how many values (9)
    addi $6, $0, 0       # R6 ← Fib(0) = 0
    sw $6, 0($1)         # MEM[R1] ← 0
    addi $1, $1, 1       # R1++
    addi $6, $6, 1       # R6 ← Fib(1) = 1
    sw $6, 0($1)         # MEM[R1] ← 1

fib_loop:
    lw $4, -1($1)        # R4 ← Fib(n-2)
    lw $5, 0($1)         # R5 ← Fib(n-1)
    add $6, $5, $4       # R6 ← Fib(n)=F(n-1)+F(n-2)
    addi $1, $1, 1       # R1++ (store next)
    addi $2, $2, 1       # R2++ (counter++)
    bne $2, $3, fib_loop # loop while counter < 9

    jrr $7              # return to caller

exit:  nop              # (halt)


```

30	addi \$3, \$0, 10	4283	R3 = 000A (= 10) ; (Next is here)
31	addi \$4, \$0, 0	4004	R4 = 0000 (= 0)
32	addi \$5, \$0, 3	40C5	R5 = 0003
33	sw \$5, 0(\$2)	6815	Memory store tested
34	addi \$4, \$4, 1	4064	Loop index update
35	addi \$2, \$2, 1	4052	
36	bne \$4, \$3, -3	7F63	
37	addi \$1, \$0, 0	4001	R1 = 0000
38	jal 2	8802	Jump to 3A; R7 = 0039h (or 883A)
39	j 24	8024	Return here: Jump back to address 0024 (C40)
3A	nop	0000	Start of Procedure
3B	xor \$2, \$2, \$2	0C92	R2 = 0000; index for iterations
3C	addi \$3, \$0, 9	4243	R3 = 0009 ; number of Fibonacci elements
3D	addi \$6, \$0, 0	4006	R6 = 0000; Clear R6
3E	sw \$6, 0(\$1)	680E	Mem[0000] = 0 ; Initially 0
3F	addi \$1, \$1, 1	4049	R1 = R1 + 1 = 0001; next memory location
40	addi \$6, \$6, 1	4076	R6 = 0001;
41	sw \$6, 0(\$1)	680E	Mem[0001] = 1 ; 2,3,5,8,13,21,34,55,89
42	lw \$4, -1(\$1)	67CC	R4 = Mem[0000] ; R4 = X_{n-2}
43	lw \$5, 0(\$1)	600D	R5 = Mem[0001] ; R5 = X_{n-1}
44	add \$6, \$5, \$4	01AC	R6 = R5 + R4 ; $X_n = X_{n-1} + X_{n-2}$
45	addi \$1, \$1, 1	4049	R1 = R1+1; next memory location
46	addi \$2, \$2, 1	4052	R2 = R2+1; increment counter index
47	bne \$2, \$3, -6	7E93	if R2 < R3, branch to instruction 41 (C69)
48	jr \$7	1E38	PC <= R7; Else Return to Address in R7 (0039)
49	nop	0000	Not executed

is being tested as illustrated in this example when the add instruction read a variable that has just been loaded.

Result:

Data memory and Register file

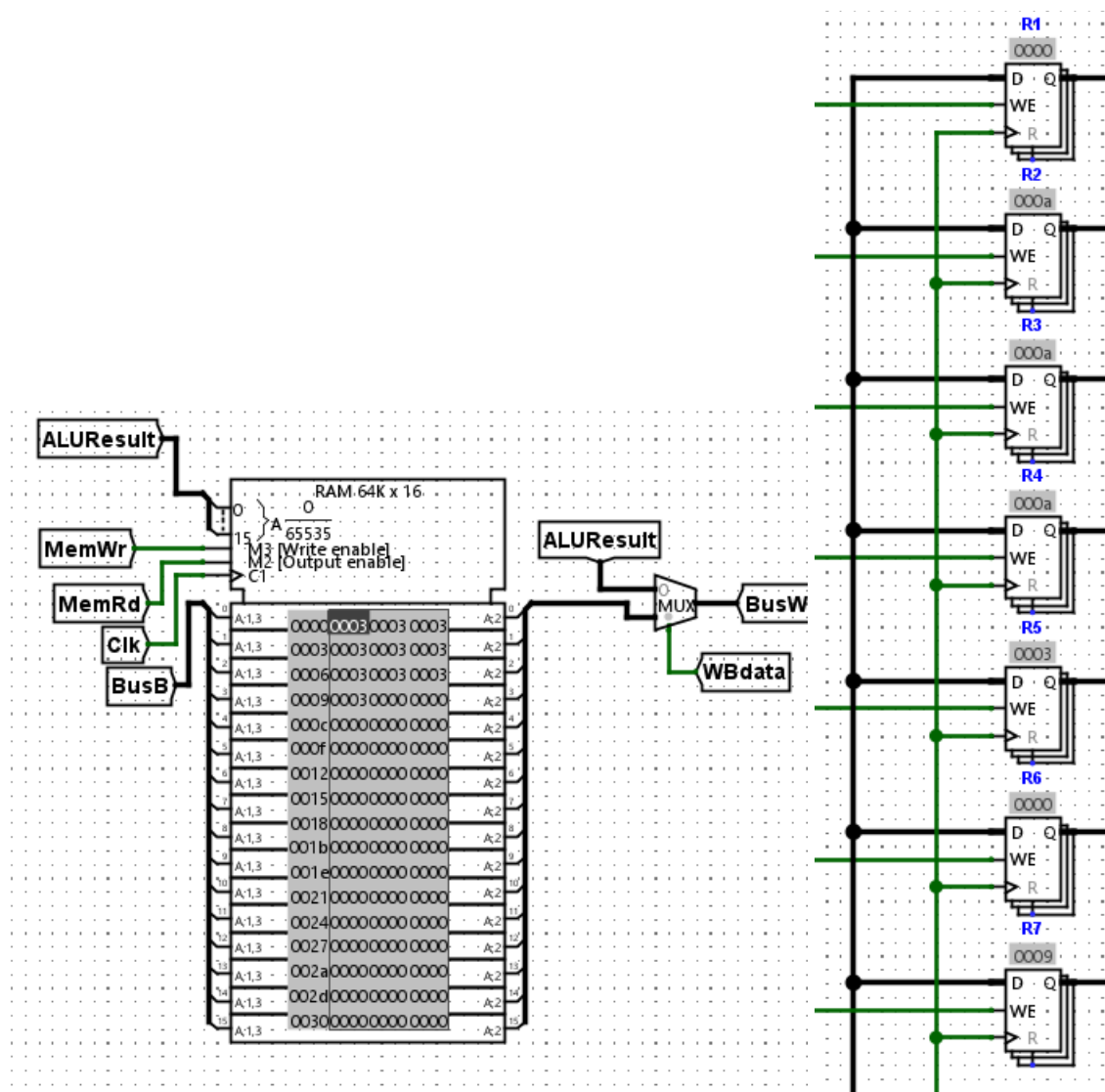

Memory Stores and Loads

- In the first loop, ten consecutive memory writes all wrote the value 3 as intended, and you saw ten corresponding MemWrite pulses.
- In the Fibonacci routine, each SW and LW accessed the right addresses—your data memory contained the sequence 0,1,1,2,3,5,8,13,21.

Loop Control with BNE

- Both the store-loop and the Fibonacci loop iterated the exact number of times (10 and 9, respectively).
- The branch unit asserted Branch only when the index was not yet equal to the limit, then de-asserted when it should have fallen through.

Arithmetic and Data Paths

- ADDI and ADD correctly initialized and updated loop counters, pointers, and the running sum.
- The ALU's add functionality produced exactly the Fibonacci sums each cycle.

Jump and Return Mechanics

- The JAL to fib saved the return PC in \$7, and the final JR used that to come back to the halt loop.

- Control signals Jump and JR fired precisely when expected.

Register File Behavior

- Registers held the right values at every stage:
 - After the store-loop, you saw R4 = 10, R2 = base+10.
 - After Fibonacci, R2 = 9, R3 = 9, and R6 = 21.

4 Conclusion

The single-cycle CPU executes the entire ISA in one clock tick, meeting project requirements for correctness across arithmetic, logic, memory, and control-flow operations. Future work could extend the design to a multi-cycle or pipelined version to improve performance.

5 References & Installing Logisim-evolution 3.9.0

- COE301 Project Specification (Term 242)
- Install Java ≥ 8 – download [from https://www.java.com](https://www.java.com).
- Go to <https://github.com/reds-heig/logisim-evolution/releases>.
- Under v 3.9.0, download logisim-evolution-3.9.0.jar.
- Open a terminal in the download folder and run
- **java -jar logisim-evolution-3.9.0.jar**
- Logisim launches; open your .circ CPU file to simulate.